This presentation describes the latest FOX Project

A low cost dedicated directional receiver for VHF and UHF fox hunts

http://www.icarc.org/icarc_foxhunt.htm

History: 102-73170 DTOA switch

Successful unit that exploits Differential Time Of Arrival technique

Uses handy-talkie (cheap Baofeng or more expensive Kenwood, Yaesu, ICOM)

DTOA

FM Receiver will demodulate a phase shift producing an audio squeal

Switch receiver input between two antennas at 500Hz to 1KHz


Orient the antenna array normal to the source to minimize audio squeal

ICARC DTOA Fox Receiver 102-73170 DTOA switch internals

555 timer to generate switching signal. A square wave of around 1KHz.

BAR63-04 PIN diode used as RF switch. Two diodes, series connected.

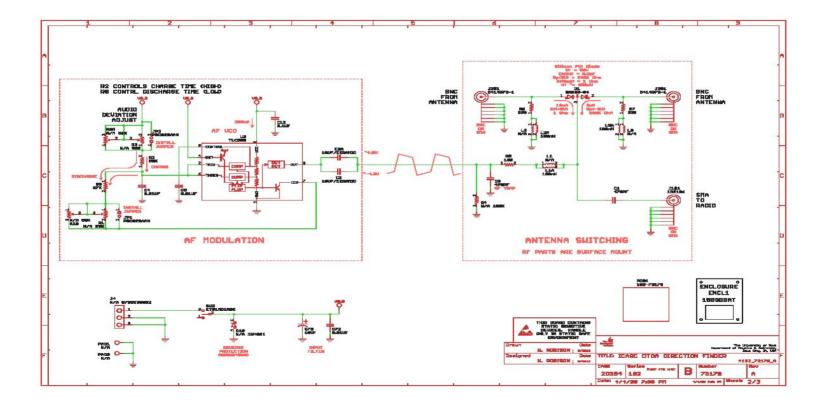Pass RF when forward biased. Only one biased at a time.




102-73185 DTOA receiver

zNEO generates switching signal. Square wave at 500Hz. BAR64-05 PIN diode used as RF switch. Two diodes, common cathode.

Pass RF when forward biased. Nominally only one diode biased at a time.

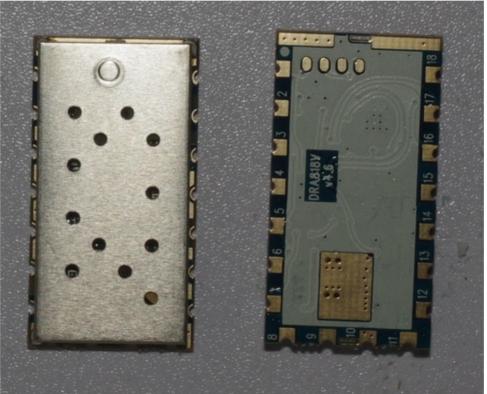ICARC DTOA Fox Receiver 102-73185 RF Section, DRA818



102-73185 RF Section DRA818/SA818 RF tranceiver Less than \$15 on ebay !!! 36mm by 19mm (1.5" by 0.750") 500mW or 1000mW output power 4V power supply

102-73185 Processor ZiLOG zNEO 128KB program FLASH 4KB data SRAM Lots of useful peripherals Free development tools (software)

ICARC DTOA Fox Receiver 102-73185 PIN Driver

MAX3188, an RS232 driver, supplies +5V or -5V on output pin

MAX870 is switch capacitor inverter.

-5V current flows only to charge node capacitance during switching.

Schematic Sheet 2:7B PIN Driver

Schematic Sheet 2:7E -5V Supply

ICARC DTOA Fox Receiver 102-73185 Audio Subsystem

DRA818 provides enable when carrier present ZNEO provides enable when it want to *talk* ZNEO uses PWM controller to implement DAC DAC bandwidth somewhat limited

> Schematic Sheet 2:2F PWM Filter Schematic Sheet 3:6D Audio Amplifier Schematic Sheet 3:3B Audio Summer

102-73185 TOY and FRAM

Same DS1672 and MB85RS4MT as used on the 102-73161 and 102-73181 Fox Transmitters

FRAM is 4Mb to make room for audio clips.

Schematic Sheet 4:5C FRAM

Schematic Sheet 2:3E TOY Clock

102-73185 Network Port ICOM CI-V compatible Full Duplex / Half Duplex

Schematic Sheet 5:4B CI-V Interface

ICARC DTOA Fox Receiver 102-73185 Display and Controls

LCD 8 characters 2 lines Rotary Encoder w/button Volume Control

Schematic Sheet 4:6D LCD Schematic Sheet 5:8D Encoder Schematic Sheet 3:4D Volume Control

ICARC DTOA Fox Receiver 102-73185 Power Management Much the same as 102-73161-25 and 102-73181 Switchmode on battery to get to 5V Linear device for 3.3VB rail.

Schematic Sheet 1:3D Switchmode power convertor Schematic Sheet 1:6D Linear Regulator Schematic Sheet 1:6D DRA818/SA818 Regulator

102-73185 Power Estimates DRA818/SA818 are power hogs Software Power Management?

Schematic Sheet 6 Power Estimates (next page)

POWER BUDGET						BATTERY CAPACITY							
	STOP	HALT	IDLE	ACTIVE									
3.3U RAIL						LR03	Vcell	Vpack	Unominal	mAH	militi	Run Tier	
U1 216F2818	1.000	1.000	5.000	18		6 CELLS	1.5	9.0	7.5	1000	7500	15H	
74LUC=4	.588	.588	.500	1		8 CELLS	1.5	12.9	10.0	1000	10000	20H	
U5 MAX878 U6/U11 MAX3188	.700 8.001	.700 8.001	.700 8.001	1 8.58		HR03							
DEVULL HMASLEE	010.01	0.001	0.001	0.00		6 CELLS	1.25	7.5	6.5	1200	7888	15H	
	2.2NA	5.2mA	6.2NA	28.5NA	VR2	8 CELLS	1.25	10.0	9.5	1288	10200	19H	
	7.25mH 11mH	17.2mH 26mH	28.5=H 31mH	67.7=H 103mH	3.3U 5.0V								
5V RAIL													
U1 DRA818	.959	.050	55	60								T I	
U1 LN4871	.956	.956	6.5	10								/	
	2.5nA 12.5=N	5.5nA 27.5=N	68nA 318nN	91nA 155nN	UR1 5.8V								
MEASURED (UNIT 1)	77.7 = A	77.7 = A	77.7 = A	77.7=0	BATT (CURRENT							
	77.7mH 77.7mH	77.7mH 77.7mH	77.7mH 77.7mH	??.?nH ??.?nH	BATT (BATT)	VOLTAGE PONER							

102-73185 T Paragraph Paragraph Paragraph Paragraph